

# How can we work with electricity?

*Interact Discovery Sheets*

Science

Years 5-8

By Allana Hiha and  
Helen Pearson

© 2010 Interact Curriculum Press

The purchasing educational institution and its staff or the purchasing individual teacher are permitted to make copies of these blackline master pages, beyond their rights under the Act, provided that:

1. The number of copies does not exceed the number reasonably required by the educational institution to satisfy its teaching purposes
2. Copies are not lent or sold
3. Every copy made clearly shows the footnote (c) Interact Curriculum Ltd. This page may be copied by the original purchaser for non-commercial use

Cover photography © R McKown | Shutterstock.com

Interact Curriculum Press  
P.O. Box 757  
Whangaparaoa, 0943  
New Zealand

[www.interactcurriculum.com](http://www.interactcurriculum.com)  
Printed and bound by CM Digital, Albany, New Zealand

ISBN 978-1-877532-75-7



# CONTENTS

3	Introduction
4	Key Competencies, Habit of Mind, Habit of Character
5	Big Idea, Key Understanding, Focus Question
6	<b>Relate</b> Jokes
7	<b>Research 1.0</b> What is electricity and where do we find it?
8	God is Powerful
9	Diagram of an Atom
10	Appliances 1
11	Appliances 2
12	Magnet Strengths
13	Making a Magnet
15	<b>Research 2.0</b> How is electricity transmitted?
16	Power Station to Lightbulb
17	Insulators, Resistors and Conductors
18	Table of Results
19	Electrical Symbols
20	Series or Parallel
21	Open or Closed
22	Setting Up Electrical Circuits
23	Electrical Circuits 1
24	Electrical Circuits 2
25	<b>Further Research</b> My Electrical Investigation
26	<b>Further Research</b> My Investigation






# INTRODUCTION

Welcome to our study of electricity, and how we make use of it. This *Interact Teacher Manual* is part of the theme, *God is peace and wants us to be peacemakers*.

What an amazing resource man discovered when he began to understand the miracle of electricity! At the touch of a switch, we have a source of power; we can carry it around with us in batteries or even tap into power sources without wires. Some think that electricity is a bit like coffee. You could live without it, but why would you want to? It has changed our lives in so many ways that we could barely begin to imagine life without it. The advances in technology that have been possible because of our ability to use electricity are no less than mindboggling.

Electricity is a form of energy and can produce light, heat and sound. To generate it, we capture the sun's rays on solar panels, harness the power of rushing water, combine chemicals or rub things together. Because we are people created in the image of God, we have the capacity to think God's thoughts after him. As lightning flashes its brilliance across the sky, or we feel, hear or see the sparks of static electricity, we are reminded that electricity was God's idea and that we are in the process of learning how to work with God's creation.

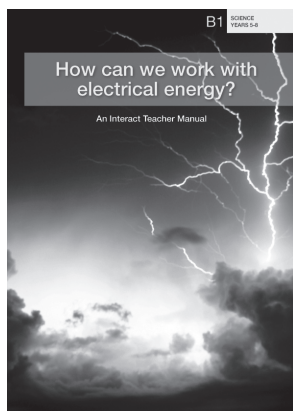The flow of electricity requires a power source and a conductor. As we focus our thoughts this term on becoming *peacemakers*, may we consider how being connected to God's power can help us to be conductors of peace.





the key competencies are:

**Relating to Others**

the habit of character focus is:

**Diplomacy**

the habit of mind focus is:

**Finding Humour**



the big idea is:

**God is Peace and  
wants us to be  
peacemakers**

the key understanding is:

**Electrical and  
magnetic energy  
can be transmitted  
and transformed  
for our use**

the focus question is:

**How can we work  
with electricity?**



# Jokes



What would you call a power failure?  
*A current event.*

A city in which no one can live?  
*Electricity.*

What did the electrician's wife say when he got home so late?  
*Wire you insulate.*

Did you know that if you learn to think about double meanings for words you can make up your own great jokes?

Read and listen to the following words and see if you can make a pun or joke by considering how they could be given a different meaning:

	ANOTHER MEANING	A WAY THE WORDS COULD BE USED TO MAKE A JOKE
wire	why are	
insulate	in so late	
conductor		
conduct		
light		
atom		
source		
bulb		
circuit		
switch		
current		
symbol		
watt		
peace		
electricity		





key areas of investigation

## **We are investigating:**

- 1.0** What is electricity and where do we find it?



# God is Powerful



God is very powerful.

Even though we can't see God, we can see the things God has done.

- God made things we can see, like \_\_\_\_\_  
\_\_\_\_\_
- God made things we can't see like \_\_\_\_\_  
\_\_\_\_\_
- Electricity is very powerful. Even though we can't see it, we can see what it does.
- Here are some of the ways electricity helps us: \_\_\_\_\_  
\_\_\_\_\_
- God made electricity. We can see what electricity does when we see lightning or when we see our hair stick to a \_\_\_\_\_
- Some electricity happens because tiny e\_\_\_\_\_ that we can't see flow through a current, just like water flows through a stream.
- At the power station, the electrons are put together and then they flow out through power lines on power poles, into w\_\_\_\_\_ that come into your home, into the power point.
- The electricity waits inside the wires in the power point until we put a p\_\_\_\_\_ in.
- Then the electricity goes into the wires in the plug, down through the wires in the lead into the wires in the heater or the lightbulb.
- The electricity makes the wires in the heater hot and the wires in the lightbulb make light.
- Isn't it clever? Why does this happen?
- It happens because G\_\_\_\_\_ is so powerful that He can make tiny electrons that we can't even see move very fast along a wire.






# Diagram of an Atom




Label the parts of the atom















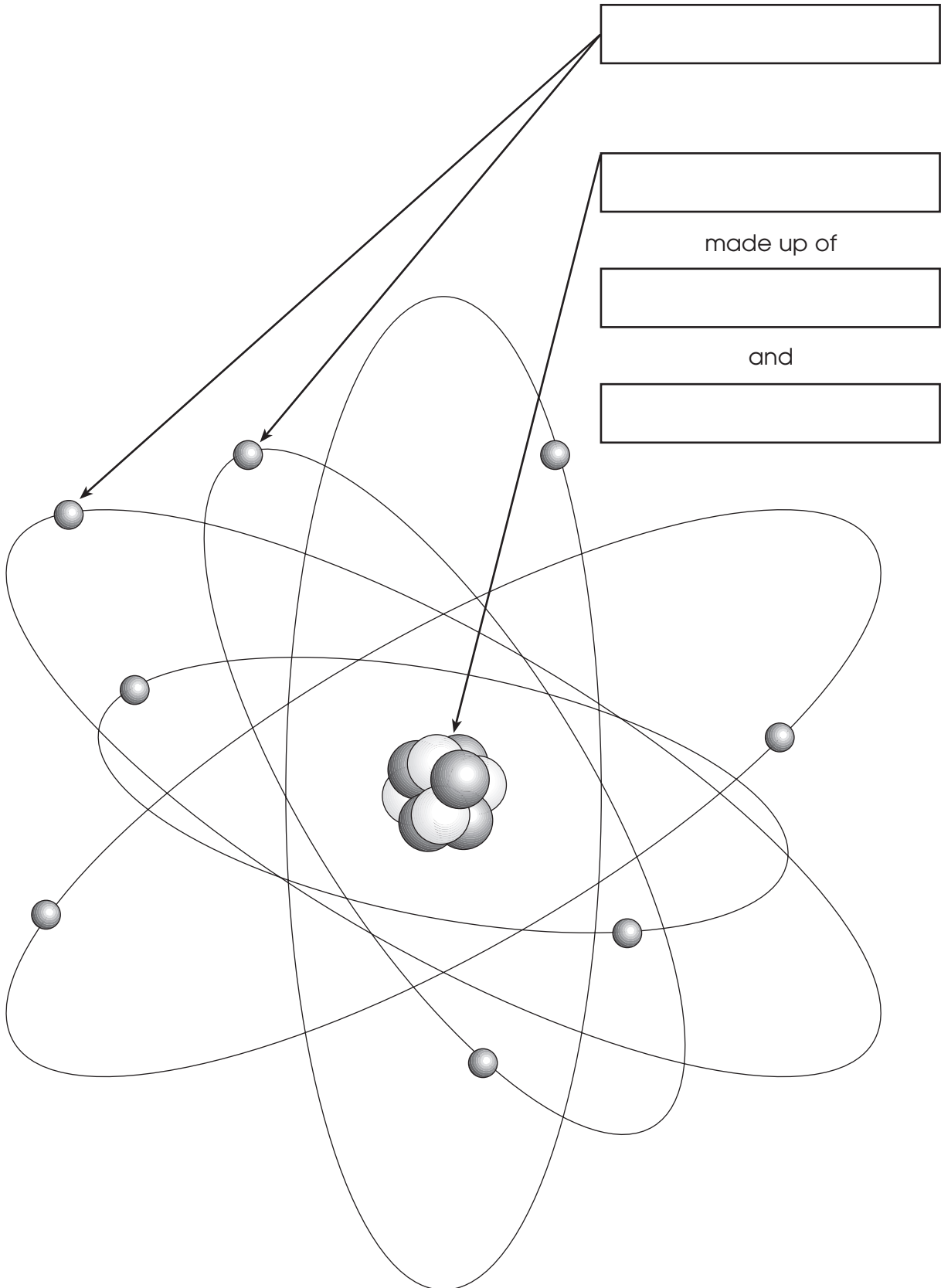


Name: \_\_\_\_\_

# Appliances 1

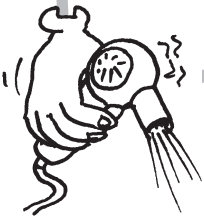

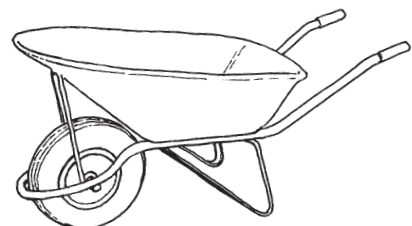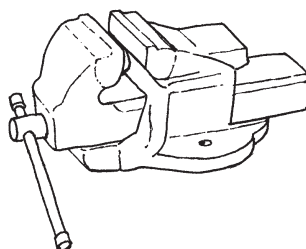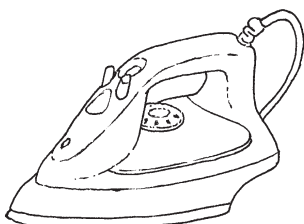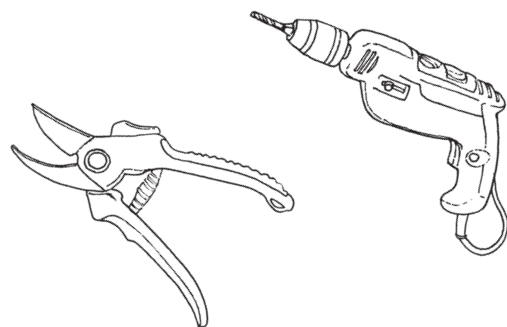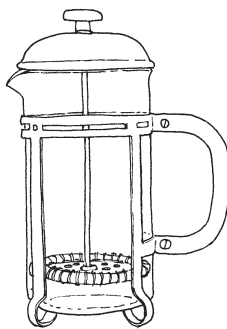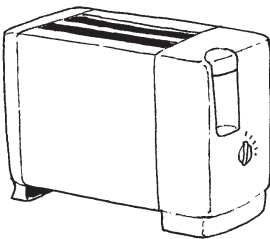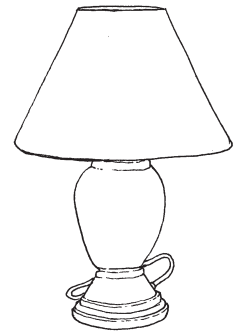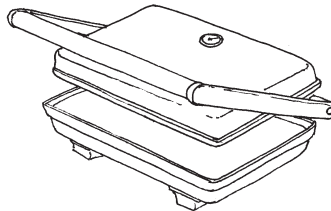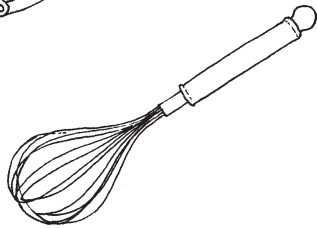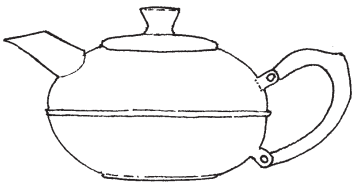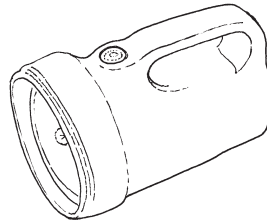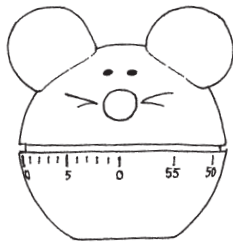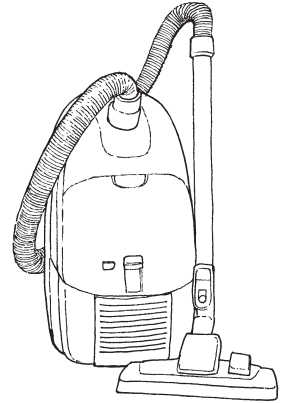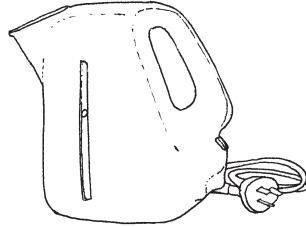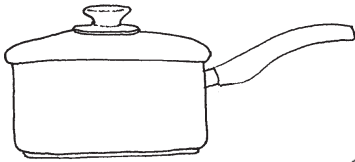Cut out the pictures and put them on the chart under the correct heading – “Objects that use electricity” or “Objects that do not use electricity”



# Appliances 2



Cut out the pictures on the separate sheet and classify them into two categories – “Objects that use electricity” and “Objects that do not use electricity”

OBJECTS THAT USE ELECTRICITY	OBJECTS THAT DO NOT USE ELECTRICITY

Name: \_\_\_\_\_



# Magnet Strengths



Complete the sentences below by underlining the correct word in the brackets


A magnet that holds (more, less) paper clips is a ( stronger, weaker) magnet.

A magnet that holds (more, less) paper clips is a (stronger, weaker) magnet.

## NOW TRY THIS


**You will need:** A selection of magnets and paper clips.

How many paper clips can a magnet hold?

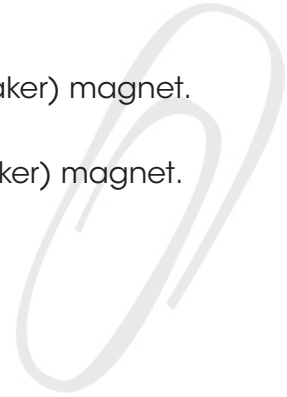

	MAGNET I USED	NO. OF PAPER CLIPS IT HELD	THIS MAGNET IS WEAK OR STRONG
1.			
2.			
3.			
4.			
5.			
6.			

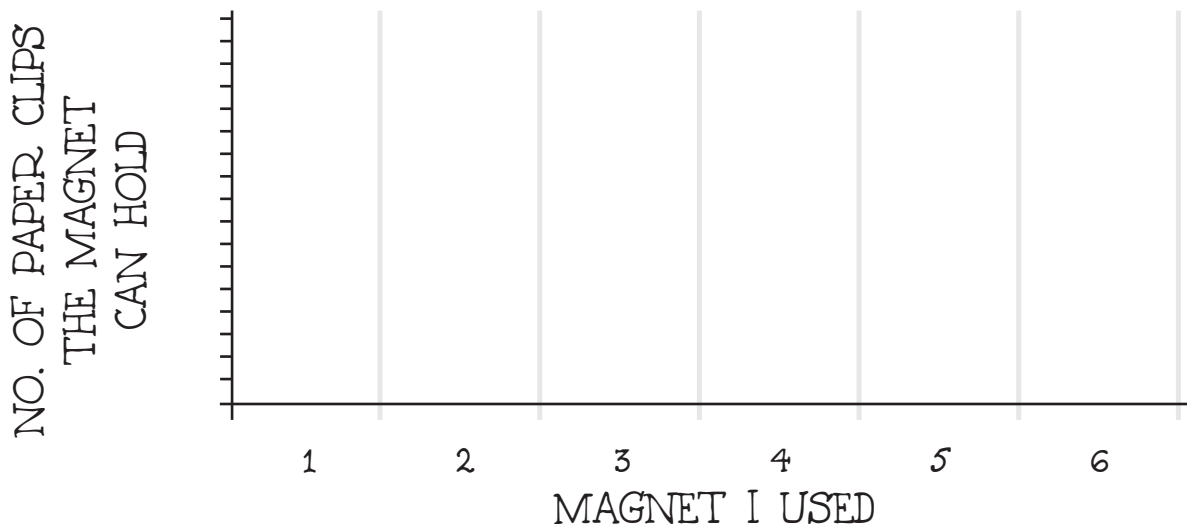Record what you have found out on a bar graph like the one below



# Making a Magnet




## You will need:

A strong magnet and a nail or paper clip.
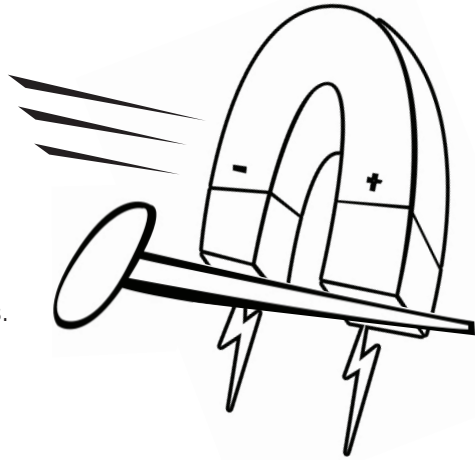
## Instructions:

Hold the magnet in your hand. Stroke the magnet along the nail (paper clip) from one end to the other. Always stroke it in the same direction. Do this ten times. Now you have your very own magnet.



My magnet can pick up

---

---

---

My magnet cannot pick up

---

---

---

Can magnets attract metal through paper, cardboard, wood or other materials? Try this out by holding a strong magnet underneath one of these materials with a metal object on the other side.

Write a few sentences about what you noticed.

---

---

---

---

Name: \_\_\_\_\_

© 2010 INTERACT CURRICULUM - THIS PAGE MAY BE COPIED BY THE ORIGINAL PURCHASER FOR NON-COMMERCIAL USE







key areas of investigation

**We are investigating:**







**2.0** How is electricity transmitted?


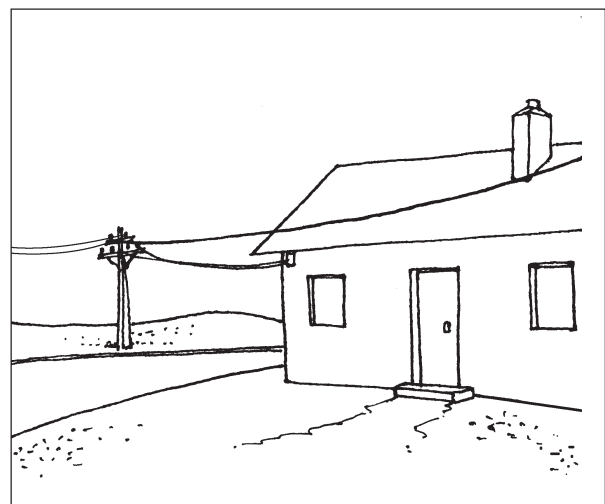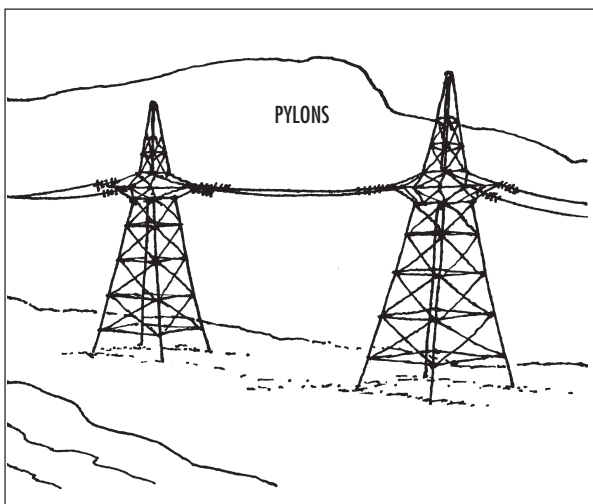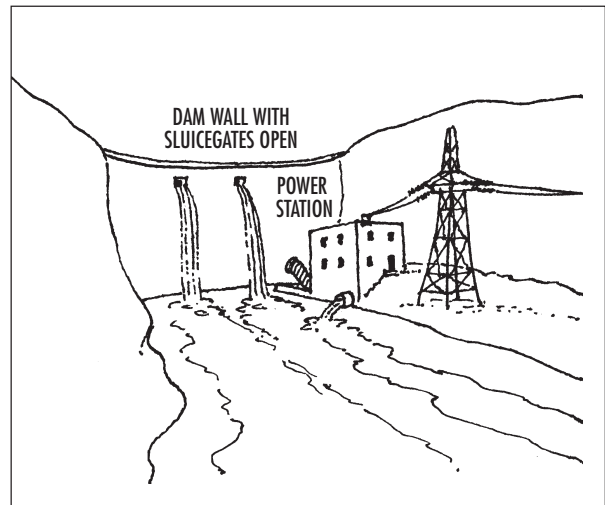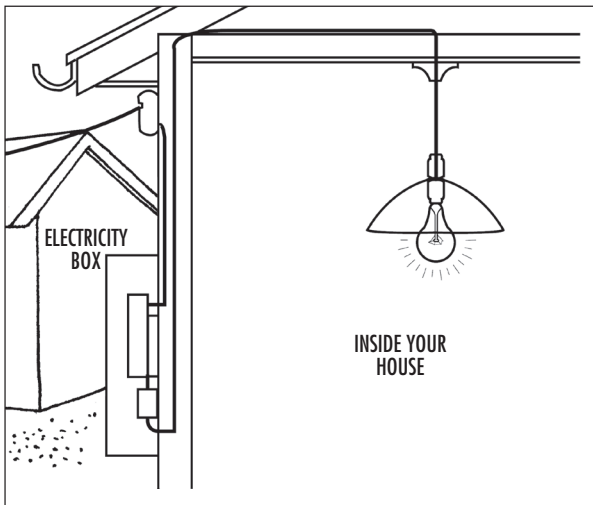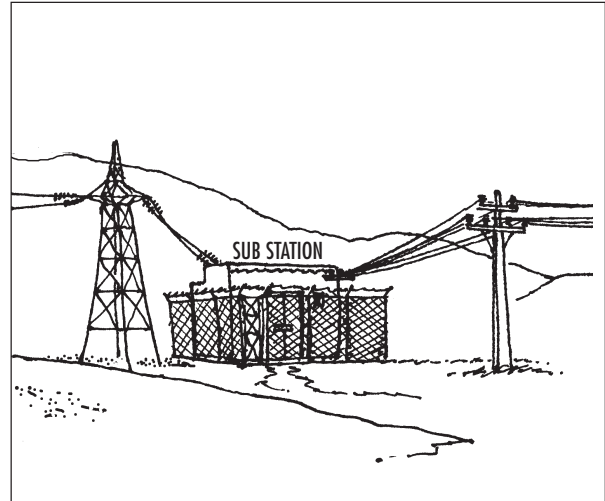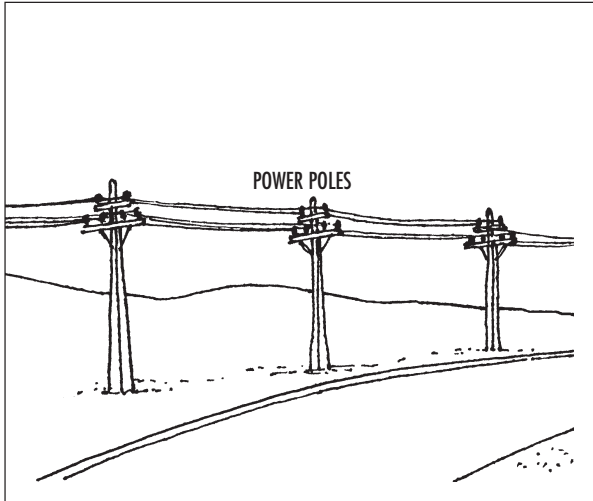
# Power Station to Light Bulb



Cut out the cards. Put them into the correct order to show how power goes from the power station to your light bulb.





# Insulators, Resistors & Conductors



## EXPERIMENT

The aim of this experiment is to find out whether different materials and objects are insulators, resistors or conductors.

An **insulator** does not conduct electricity.

A **resistor** allows some electricity through, but resists its path.


A **conductor** does conduct electricity, allowing electricity to flow through it freely.

Set up the circuit shown, without any test material in the circuit. Close the switch and observe how bright the bulb is. Now set up the circuit, putting the material you are going to test into the marked place on the diagram using alligator clips. Close the switch and observe the light bulb. This will tell you how well the material conducts electricity.


If the light bulb **does not go on**, it is an **insulator**.

If the bulb is **dim**, it is a **resistor**.

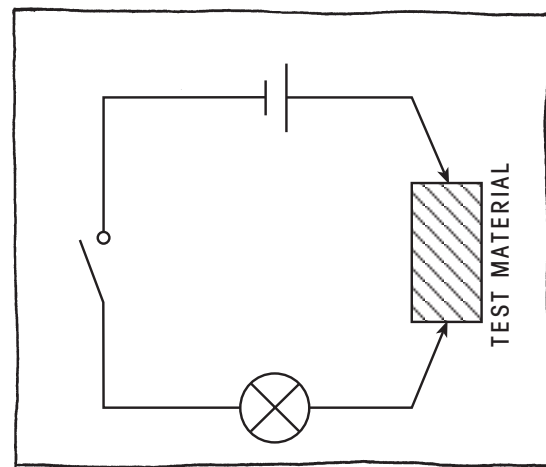If the bulb is **bright**, it is a **conductor**.



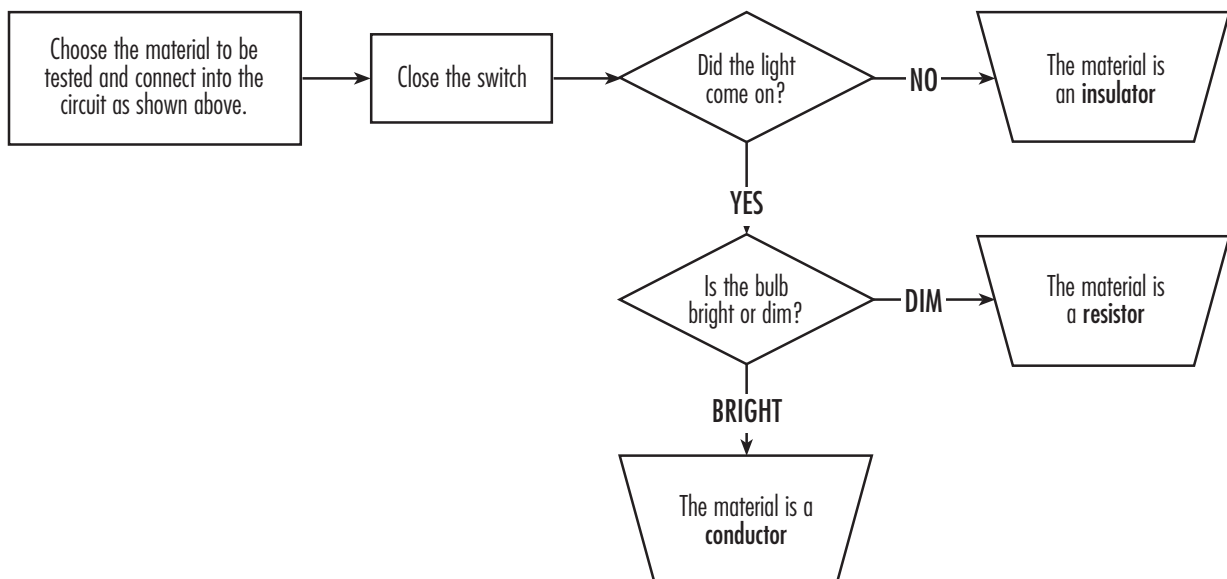Use the flow diagram below to determine whether the material is an insulator, a resistor or a conductor. Write the results on the table on the next page.














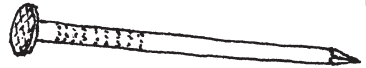


Name: \_\_\_\_\_



# Table of Results



Fill in the table below using the results from your experiment.  
Put a tick in the box that shows what the material is – an **insulator**,  
a **resistor** or a **conductor** of electricity.

MATERIAL	INSULATOR	RESISTOR	CONDUCTOR
WOOD 			
CLOTH 			
NAIL 			
PLASTIC RULER 			
TIN FOIL 			
COPPER 			
PAPER 			
METAL PAPER CLIP 			
RUBBER 			
LEAD IN A PENCIL 			
ALUMINIUM 			
WIRE 			
SCISSORS 			
FORK 			



# Electrical Symbols




Link each symbol with the correct word.



Lamp



Closed Switch

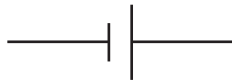

Battery




Wire



Open Switch

Link each symbol with the correct word.

LAMP	BATTERY		OPEN SWITCH	
		_____		

Name: \_\_\_\_\_




# Series or Parallel



Write down whether each circuit is set up in **series** or in **parallel**.


1.

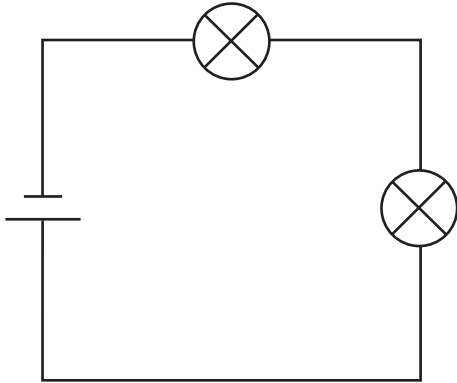

This circuit is in

\_\_\_\_\_


2.

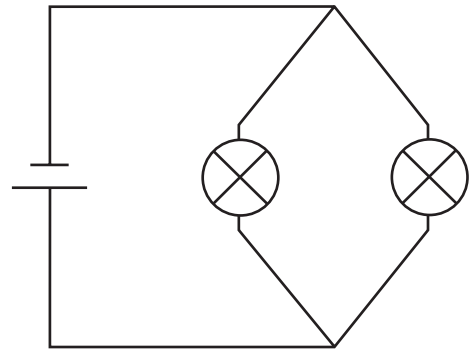

This circuit is in

\_\_\_\_\_


3.

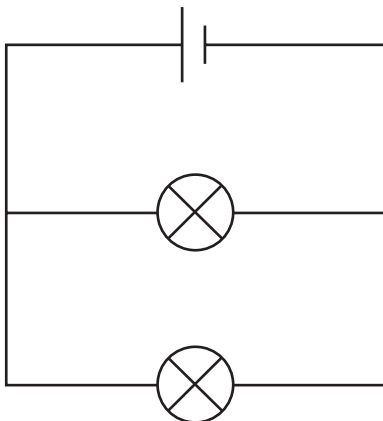

This circuit is in

\_\_\_\_\_


4.

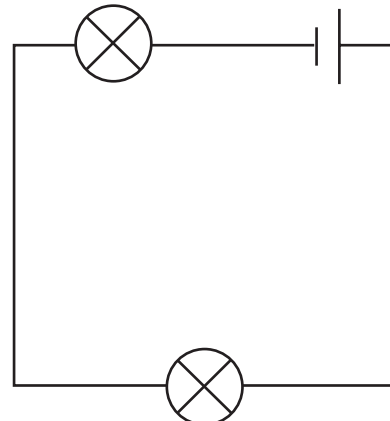

This circuit is in

\_\_\_\_\_


5.

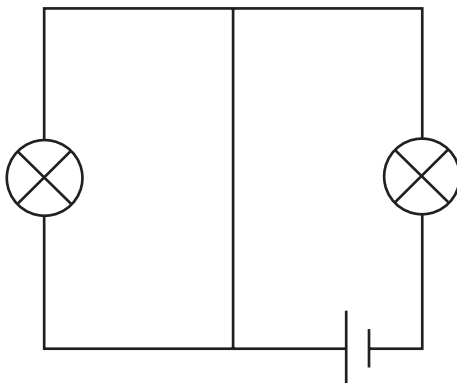

This circuit is in

\_\_\_\_\_

6.

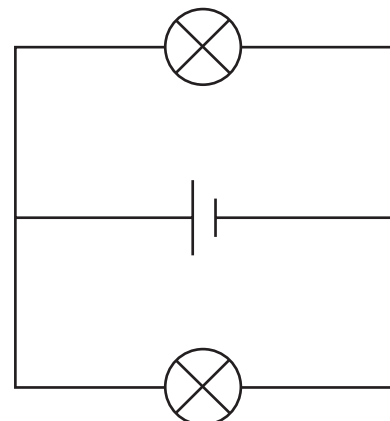

This circuit is in

\_\_\_\_\_




# Open or Closed



Look at each circuit and decide whether it is an open circuit or a closed circuit. Write your answer under each circuit.

Ask yourself "Will this circuit work?" A closed circuit will let the electrons run through it and so the appliances (lamps, etc) in the circuit will work.


1.

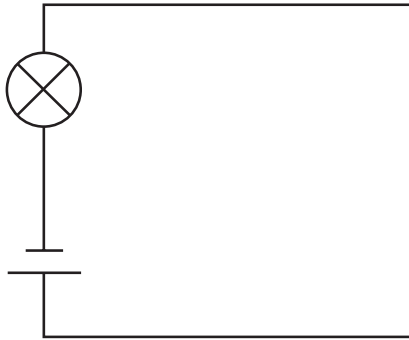

\_\_\_\_\_

\_\_\_\_\_


2.

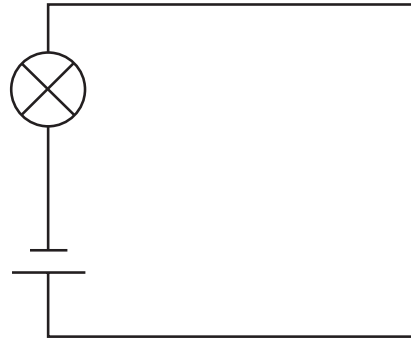

\_\_\_\_\_

\_\_\_\_\_

3.

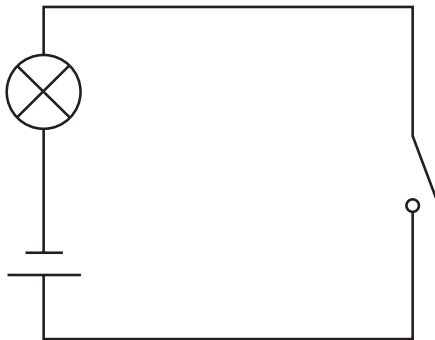

\_\_\_\_\_

\_\_\_\_\_


4.



\_\_\_\_\_

\_\_\_\_\_


5.

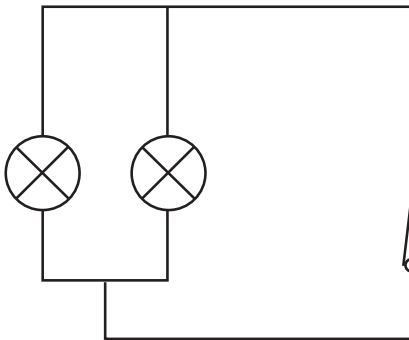

\_\_\_\_\_

\_\_\_\_\_

6.

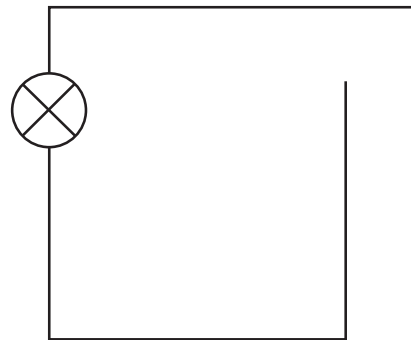

\_\_\_\_\_

\_\_\_\_\_

Name: \_\_\_\_\_



# Setting Up Electrical Circuits



Read the instructions, then set up the circuit and write your results.

1. Set up a circuit with a battery, a closed switch and 1 lamp.

**Results:** \_\_\_\_\_

---

---

---

---

Draw the circuit you set up:

---

---

---

---

2. Set up a circuit with a battery, a closed switch and 2 lamps.

**Results:** \_\_\_\_\_

---

---

---

---

Draw the circuit you set up:

---

---

---

---

3. Set up a circuit with a battery, and 2 lamps in parallel.

**Results:** \_\_\_\_\_

---

---

---

---

Draw the circuit you set up:

---

---

---

---

4. Set up a circuit with a battery, 2 lamps in series and 1 in parallel. Put a switch between the lamps in series and the lamp in parallel. Have the switch open.

**Results:** \_\_\_\_\_

---

---

---

---

Draw the circuit you set up:

---

---

---

---

5. Close the switch in the circuit you set up in 4.

**Results:** \_\_\_\_\_

---

---

---

---

Draw the circuit you set up:

---

---

---

---





# Electrical Circuits 1



Below are some circuits for you to set up. After you have set up each one, close the switch and look at what happens. Write down your results and answer the questions.

1. Results: \_\_\_\_\_

\_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

2. Results: \_\_\_\_\_

\_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

Were the lamps in this circuit the **same brightness / brighter / not as bright** as the lamp in circuit 1?

\_\_\_\_\_

Are these lamps in **series** or in **parallel**?

\_\_\_\_\_

What happened when the switch was **open**?

\_\_\_\_\_

What happened when you **closed** the switch?

\_\_\_\_\_

3. Results: \_\_\_\_\_




\_\_\_\_\_  
\_\_\_\_\_

Were the lamps in this circuit the **same brightness / brighter / not as bright** as the lamp in circuit 1?

\_\_\_\_\_

Are these lamps in **series** or in **parallel**?

\_\_\_\_\_

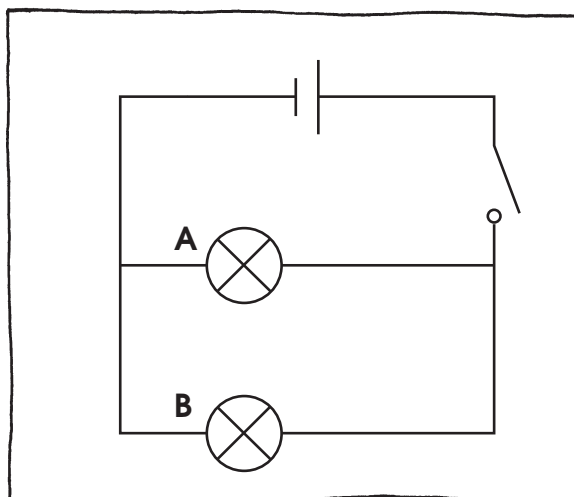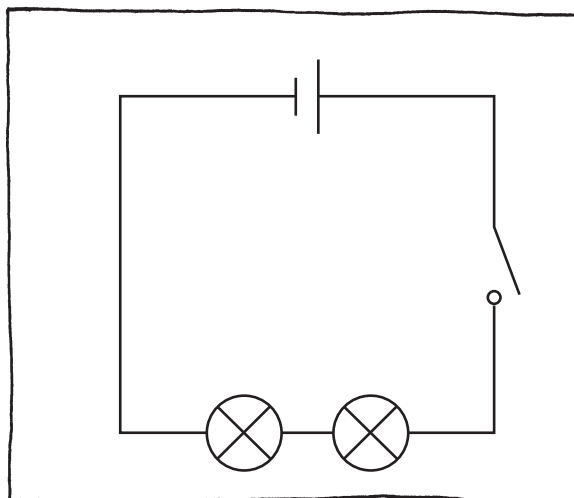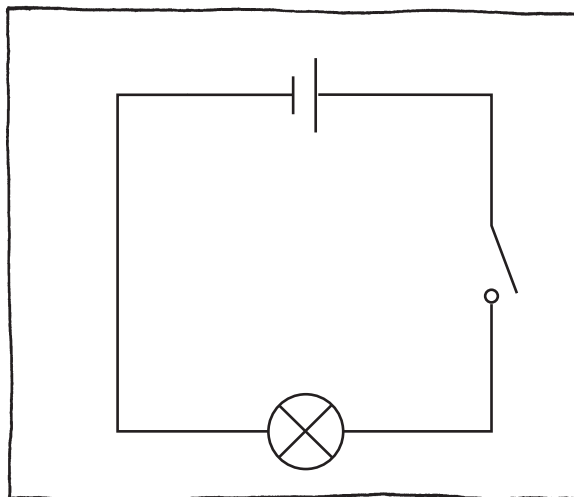

Name: \_\_\_\_\_




# Electrical Circuits 2



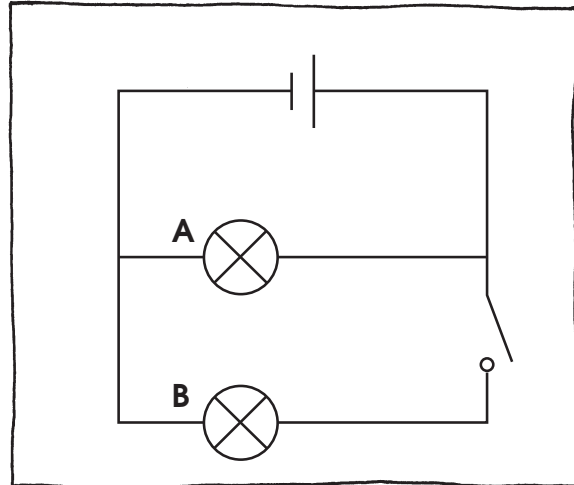4. Results: \_\_\_\_\_

What happened when the **switch** was **open**?



What happened when the **switch** was **closed**?



5. Results: \_\_\_\_\_

Which lamp is the **brightest** when the **switch** is closed – A, B or C?

Which two lamps are in series?

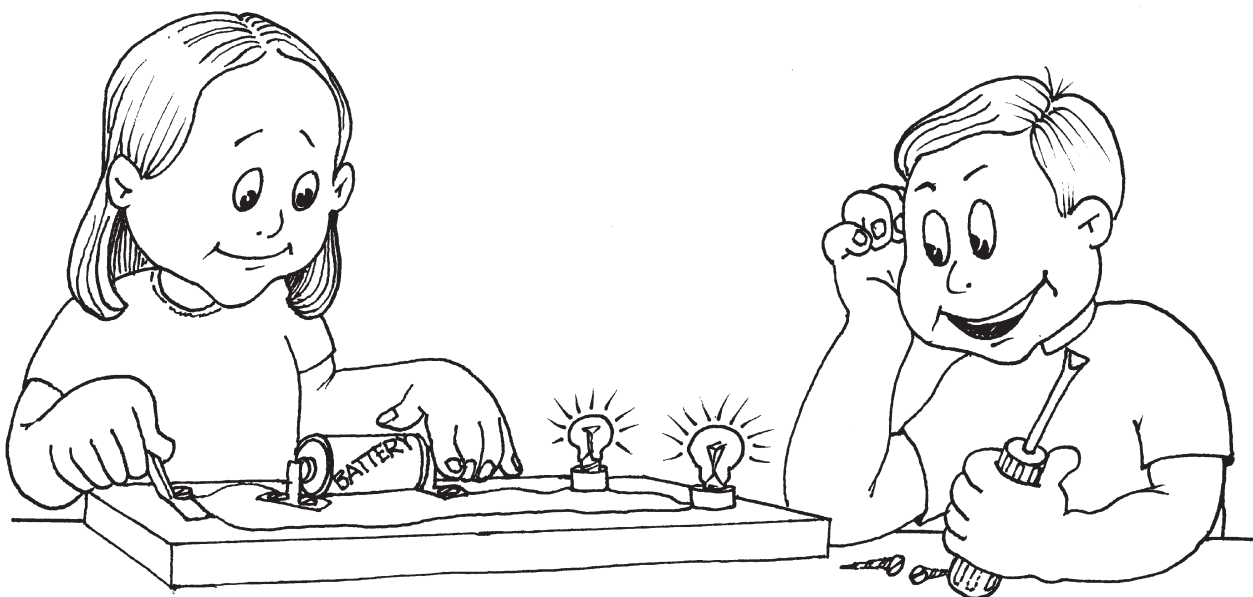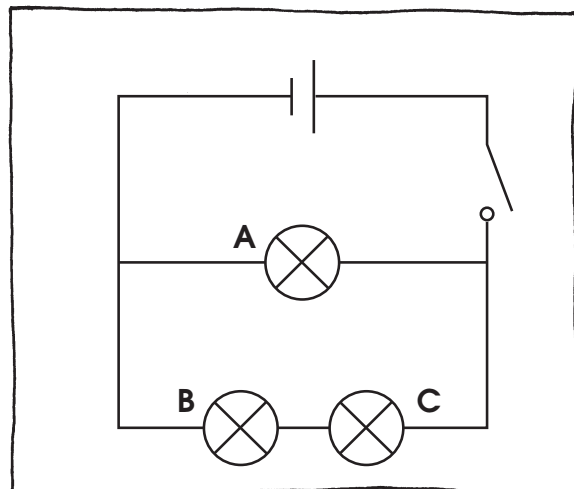



# My Electrical Investigation



Use the plan below to help you investigate electricity e.g.

- which metal will conduct electricity most and least efficiently
- which metal will be best for an electric fence post  
(place them in a line according to your estimation and then test)
- which brand of battery lasts the longest

Consider why the information that you gained is useful information for a particular situation.

What I'd like to find out about electricity
What I already know to help with my investigation
How I will investigate it
What I predict will happen
What actually happened
My conclusion is that
Further investigation: How can I use what I have learnt OR How can I find out more about electricity

Name: \_\_\_\_\_

© 2010 INTERACT CURRICULUM - THIS PAGE MAY BE COPIED BY THE ORIGINAL PURCHASER FOR NON-COMMERCIAL USE



# My Investigation



Use the plan below to help you carry out an investigation about sound.

I want to find out \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

What I already know \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

Steps I need to follow to carry out my investigation \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

What I predict will happen \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

What actually happened \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

My conclusion \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

How can I apply what I've learnt in this investigation? \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

Questions for further research \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_